

ELECTRICAL ENGINEERING

Q.13 The complete set of only those Logic Gates designated as Universal Gates is

- (A) NOT, OR and AND Gates
- (B) XNOR, NOR and NAND Gates
- (C) NOR and NAND Gates
- (D) XOR, NOR and NAND Gates